

Kel in Vo:
$$3V_0 + 3V_1 + \frac{V_0 - V_1}{2S} + 2V_0 = 0 \implies V_0 \left(3 + \frac{1}{2S} + 2\right) = V_1 \left(-3 + \frac{1}{2S}\right)$$

$$= > V_1 = \frac{5 + \frac{1}{2S}}{-3 + \frac{1}{2S}} V_0 = \frac{10S + 1}{-6S + 1} V_0 \left(\frac{11}{2S}\right) \xrightarrow{\text{in (II)}} > \left(\frac{10S + 1}{-6S + 1}\right) \left(S + \frac{1}{2S}\right) V_0 + V_0 \left(-2 - \frac{1}{2S}\right) = \left[S + \frac{1}{2S}\right] = \frac{V_0}{I_S} = \frac{V_0}{I_S}$$

#3

$$I_{s}$$
 I_{s}
 I_{s}

$$\frac{I_{0}=I_{S}, I_{B}=2V_{0}=\frac{2}{3}(I_{C}-I_{A})}{I_{A}=3V_{1}=\frac{3}{3}(I_{0}-I_{C})} > 25(I_{C}+\frac{2}{3}(I_{C}-I_{A}))+\frac{1}{3}(I_{C}-\frac{3}{3}(I_{0}-I_{C}))+\frac{1}{5}(I_{C}-I_{0})$$

=>
$$2SI_{c} + \frac{4}{3}SI_{c} - \frac{4}{3}SI_{A} + \frac{1}{3}I_{c} - \frac{1}{5}I_{D} + \frac{1}{5}I_{C} + \frac{1}{5}I_{C} - \frac{1}{5}I_{D} = 0$$

$$I_{c}(2S + \frac{4}{3}S + \frac{1}{3} + \frac{1}{5} + \frac{1}{5}) - I_{s}(\frac{1}{5} + \frac{1}{5}) = \frac{4}{3}S(\frac{3}{5}(I_{D} - I_{c}))$$


$$I_{c}(2S + \frac{4}{3}S + \frac{1}{3} + \frac{1}{5} + \frac{1}{5} + 12) = I_{s}(\frac{1}{5} + \frac{1}{5} + 4) \xrightarrow{I_{c} = I_{o}}$$

$$H = \frac{I_{o}}{I_{c}} = \frac{3(2 + 4S)}{I_{c}}$$

$$H = \frac{L_0}{L_S} = \frac{3(2+4S)}{65^2+6+49S}$$
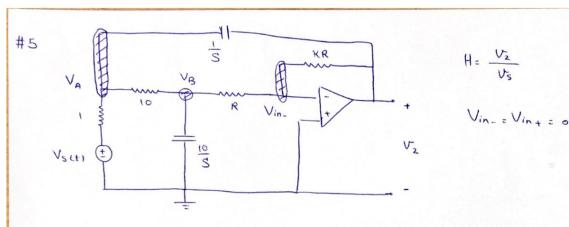
#4

$$V_{S_1} = \frac{V_1}{10}$$
 $V_{S_2} = \frac{V_2}{2}$
 $V_{S_3} = \frac{V_1}{10}$
 $V_{S_4} = \frac{V_2}{2}$
 $V_{S_5} = \frac{V_1}{10}$
 $V_{S_4} = \frac{V_2}{2}$
 $V_{S_5} = \frac{V_1}{10}$
 $V_{S_4} = \frac{V_2}{2}$
 $V_{S_5} = \frac{V_1}{10}$
 $V_{S_5} = \frac{V_1}{10}$
 $V_{S_6} = \frac{V_1}{10}$
 V_{S



$$KcL \text{ in } V_{A}: \frac{V_{A}-V_{2}}{\frac{1}{S}} + \frac{V_{A}-V_{B}}{10} + \frac{V_{A}-V_{S}}{1} = 0 \implies V_{A} \left(S + \frac{11}{10}\right) - SV_{2} - \frac{V_{B}}{10} = V_{S}$$

$$KcL \text{ in } V_{B}: \frac{V_{B}-V_{A}}{10} + \frac{V_{B}-V_{in}}{R} + \frac{S}{10}V_{B} = 0 \implies V_{A}: V_{B} \left(1 + S - \frac{10}{R}\right)$$

$$(1)$$

$$KCL in Vin : \frac{0 - VB}{R} + \frac{0 - V_2}{KR} = 0 = S \frac{VB}{K} = \frac{V_2}{KR} = S \frac{V_2}{K}$$
 (III)


$$\stackrel{(\underline{\Pi}) : n(\underline{\Pi})}{\longrightarrow} V_{A} = \frac{V_{2}}{K} \left(1 + S - \frac{10}{R} \right) (\underline{IV}) \xrightarrow{in(\underline{I})}$$

$$(1+S-\frac{10}{R})(S+\frac{11}{10})\frac{U_2}{K}-SV_2-\frac{1}{10K}U_2=U_3=YH=\frac{V_2}{V_3}=\frac{10RK}{10SR+21SR-10SRK+10R}$$

$$R=1 \rightarrow 10S^{2} + 218S - 10SK + 10 - 100S - 110 = 0$$
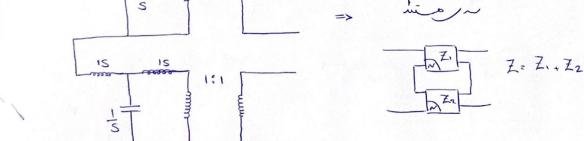
$$= \rightarrow K = \frac{10S^{2} - 79S - 100}{10S}$$





$$Z_{12} = \frac{y}{I_2}\Big|_{I_1 = 0} = \frac{1}{S}$$
 \Rightarrow $Z_1 = \begin{bmatrix} \frac{1}{S} & \frac{1}{S} \\ \frac{1}{S} & \frac{1}{S} \end{bmatrix}$

$$V_{1} = SI_{1} + \frac{1}{5} (I_{1} + I_{2})$$

$$V_{2} = SI_{1} + \frac{1}{5} (I_{1} + I_{2})$$

$$V_{3} = SI_{1} + \frac{1}{5} (I_{1} + I_{2})$$

$$V_{4} = SI_{1} + \frac{1}{5} (I_{1} + I_{2})$$

$$V_{5} = \frac{V_{1}}{I_{1}} \Big|_{I_{1}=0} = \frac{1}{5}$$

$$Z_{11} = \frac{V_{1}}{I_{1}} \Big|_{I_{1}=0} = S + \frac{1}{5}$$

$$\Rightarrow Z_{2} \begin{bmatrix} s + \frac{1}{5} & \frac{1}{5} \\ \frac{1}{5} & s + \frac{1}{5} \end{bmatrix} \Rightarrow Z = \begin{bmatrix} s + \frac{1}{5} & \frac{1}{5} \\ \frac{1}{5} & s + \frac{1}{5} \end{bmatrix} + \begin{bmatrix} \frac{1}{5} & \frac{1}{5} \\ \frac{1}{5} & \frac{1}{5} \end{bmatrix} = \begin{bmatrix} \frac{s^{2}+2}{5} & \frac{2}{5} \\ \frac{2}{5} & \frac{s^{2}+2}{5} \end{bmatrix}$$

#2
$$V_{s} \stackrel{I_{1}}{\rightleftharpoons} V_{1} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \qquad Z_{out} = Z_{22} = \frac{\overline{V_{2}}}{I_{2}} \Big|_{\Sigma_{1}=0}$$

$$V_{1} = Z_{11} I_{1} + Z_{12} I_{2}$$
 (I) duailys sing $Z_{1} = Z_{1} I_{1} + Z_{12} I_{2}$ (II) $Z_{2} = Z_{21} I_{1} + Z_{22} I_{2}$ (II) $Z_{2} = Z_{21} I_{1} + Z_{22} I_{2}$ (II)

#4 +
$$\frac{1}{20}$$
 $\frac{1}{20}$
 $\frac{1}{20}$

kd in
$$V_2: \frac{\dot{V_2} - \dot{V_1}}{4} + 0.5 \dot{V_1} + \frac{\dot{V_2}}{8} - \dot{I}_2 = 0 = > \dot{V_2} \left(\frac{1}{4} + \frac{1}{8} \right) = \dot{I}_2 + \dot{V}_1 \left(-\frac{1}{2} + \frac{1}{8} \right)$$

$$= > \dot{V_2} = \frac{8}{3} \dot{I}_2 - \dot{V}_1 \quad \text{(II)} \qquad \stackrel{\text{incl}}{\longrightarrow} \dot{V}_1 \left(\frac{3}{10} + \frac{1}{10} \dot{j} \right) - \frac{7}{20} \left(\frac{8}{3} \dot{I}_2 - \dot{V}_1 \right) = \dot{I}_1$$

$$= > \dot{V}_1 \left(\frac{13}{20} - \frac{1}{10} \dot{j} \right) = \frac{14}{15} \dot{I}_2 + \dot{I}_1 \implies \dot{V}_1 = \left(\frac{728}{519} + \dot{j} \frac{112}{519} \right) \dot{I}_2 + \left(\frac{260}{173} + \dot{j} \frac{40}{173} \right) \dot{I}_1$$

$$\dot{V}_2 \left(\frac{41}{20} - \dot{j} \frac{7}{20} \right) = \frac{8}{3} \dot{I}_2 - (3 - \dot{j}) \dot{I}_1 = > \dot{V}_2 = \left(\frac{656}{519} + \dot{j} \frac{112}{519} \right) \dot{I}_2 + \left(\frac{-260}{173} + \dot{j} \frac{40}{173} \right) \dot{I}_1$$

$$= \times Z = \begin{bmatrix} \frac{260}{173} + j \frac{40}{173} & \frac{728}{519} + j \frac{112}{519} \\ \frac{-260}{173} + j \frac{40}{173} & \frac{656}{519} + j \frac{112}{519} \end{bmatrix}$$

#6

$$V_1$$
 V_2
 V_1
 V_2
 V_1
 V_2
 V_3
 V_4
 V_2
 V_1
 V_1
 V_2
 V_1
 V_2
 V_1
 V_2
 V_1
 V_2
 V_1
 V_1
 V_2
 V_1
 V_2
 V_1
 V_1
 V_2
 V_1
 V_1
 V_2
 V_1
 V_2
 V_1
 V_2
 V_1
 V_2
 V_1
 V_2
 V_1
 V_1
 V_2
 V_1
 V_1
 V_2
 V_1
 V_2
 V_1
 V_1
 V_2
 V_1
 V_2
 V_1
 V_2
 V_1
 V_2
 V_1
 V_2
 V_1
 V_2
 V_1
 V_1
 V_2
 V_1
 V_1
 V_2
 V_1
 V_2
 V_1
 V_1
 V_1
 V_2
 V_1
 V_2
 V_1
 V_2
 V_1
 V_1
 V_1
 V_2
 V_1
 V_1
 V_2
 V_1
 V_1
 V_2
 V_1
 V_1
 V_1
 V_2
 V_1
 V_1
 V_2
 V_1
 V_1
 V_1
 V_2
 V_1
 V_1
 V_1
 V_1
 V_2
 V_1
 V_1
 V_1
 V_1
 V_1
 V_1
 V_1
 V_1
 V_2
 V_1
 V_1

$$\begin{bmatrix} \frac{1}{2} + 2 + 3 - 1 \\ -2 + 1 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ -2 + 1 \end{bmatrix}$$


$$= \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$= \begin{bmatrix} \frac{q}{2} & -1 \\ 0 & 5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$$

$$= \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ 0 \end{bmatrix}$$

$$\begin{cases}
\frac{q}{2}V_1 - V_2 = 1 & \longrightarrow & \frac{q}{2}V_1 = 1 \Rightarrow V_1 = \frac{z}{q}
\end{cases}$$

$$5V_2 = 0 \longrightarrow V_2 = 0$$

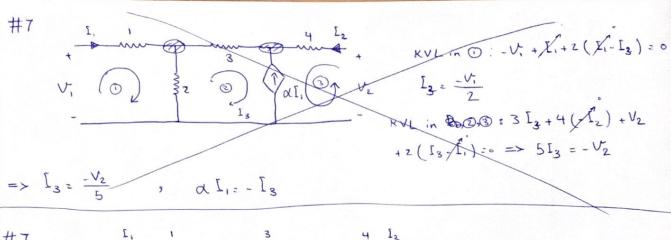

#7

$$I_1$$
 I_2
 I_3
 I_2
 I_2
 I_2
 I_2
 I_2
 I_2
 I_2
 I_3
 I_2
 I_3
 I_2
 I_3
 I_4
 I_2
 I_2
 I_3
 I_4
 I_2
 I_2
 I_3
 I_4
 I_2
 I_4
 I_2
 I_4
 I_2
 I_4
 I_4
 I_4
 I_5
 I_7
 I_8
 I_8

KVL in $I_{1}: -V_{1} + I_{1} + 2(I_{1} + I_{3}) = -2I_{3} = -2I_$

$$\Rightarrow 9 \int_{2} + (2.5\alpha) \left(\frac{1}{3(1 + \frac{2}{3}\alpha)} V_{1} - \frac{2}{3(1 + \frac{2}{3}\alpha)} I_{2} \right) = V_{2}$$

$$\Rightarrow \int_{2} \left(9 - \frac{2(2.5\alpha)}{3(1 + \frac{2}{3}\alpha)} \right) = -\frac{(2.5\alpha)}{3(1 + \frac{2}{3}\alpha)} V_{1} + V_{2} \implies \left[I_{2} - \frac{2.5\alpha}{8\alpha + 23} V_{1} + \frac{3.2\alpha}{8\alpha + 23} V_{2} \right]$$

$$\Rightarrow I_{2} = \frac{V_{2}}{9} - \frac{I_{1}}{9} \left(2 + 5\alpha \right) \implies I_{1} = \frac{1}{3(1 + \frac{2}{3}\alpha)} V_{1} - \frac{2}{3(1 + \frac{2}{3}\alpha)} \left(\frac{V_{2}}{9} - \frac{I_{1}}{9} (2 + 5\alpha) \right)$$

$$\Rightarrow I_{1} \left(1 - \frac{1}{3(1 + \frac{2}{3}\alpha)} \left(\frac{2}{9} (2 + 5\alpha) \right) \right) = \frac{U_{1}}{3(1 + \frac{2}{3}\alpha)} - \frac{2V_{2}}{27(1 + \frac{2}{3}\alpha)}$$

$$\Rightarrow I_{1} = \frac{9}{8\alpha + 23} V_{1} - \frac{2}{8\alpha + 23} V_{2} = Y = \begin{bmatrix} \frac{9}{8\alpha + 23} & \frac{-2}{8\alpha + 23} \\ \frac{-2.5\alpha}{8\alpha + 23} & \frac{3.2\alpha}{8\alpha + 23} \end{bmatrix}$$

$$\det(Y) = 0 \implies \frac{1}{8x + 23} = 0 ???$$

#8

Gs
$$f_{1}$$
 V_{2}
 V_{3}
 V_{4}
 V_{5}
 V_{7}
 V_{7}
 V_{7}
 V_{8}
 V_{8}
 V_{8}
 V_{8}
 V_{9}
 V_{1}
 V_{1}
 V_{1}
 V_{2}
 V_{2}
 V_{1}
 V_{2}
 V_{2}
 V_{2}
 V_{2}
 V_{3}
 V_{4}
 V_{1}
 V_{2}
 V_{2}
 V_{2}
 V_{3}
 V_{4}
 V_{5}
 V_{7}
 V_{7}
 V_{7}
 V_{7}
 V_{7}
 V_{7}
 V_{7}
 V_{7}
 V_{7}
 V_{8}
 $V_{$

KUL in ①: -V₁ =
$$\frac{1}{2}$$
 [1; + $\frac{1}{3}$ (1; + $\frac{1}{2}$) = 0

 $\frac{1}{2}$ S

 $V_1 = \frac{5}{6}$ [1; + $\frac{1}{3}$ [2] (1)

KVL in (2):
$$-V_2 + \frac{1}{2S} \left(I_2 + \frac{1}{2} I_1 \right) + \frac{1}{3} \left(I_1 + I_2 \right) = 0$$

$$\Rightarrow I_{2}\left(\frac{1}{2S} + \frac{1}{3}\right) = V_{2} \left\{-1, \left(\frac{1}{3} + \frac{1}{4S}\right)\right\} \Rightarrow I_{2} = \frac{6S}{2S+3} \left\{V_{2} - \frac{4S+3}{2(3+2S)}\right\}. \tag{II}$$

$$\frac{(II) in (I)}{> V_{1} = \frac{5}{6} I_{1} + \frac{1}{3} \left(\frac{65}{25+3} V_{2} - \frac{45+3}{6+45} I_{1} \right) => V_{1} = \left(\frac{5}{6} - \frac{45+3}{3(45+6)} \right) I_{1} + \frac{25}{25+3} V_{2}$$

$$\frac{-525+93}{6} = 25 - 25 - 25$$

$$=> H = \begin{bmatrix} \frac{525+93}{30(25+3)} & \frac{25}{25+3} \\ \frac{-45-3}{2(3+25)} & \frac{65}{25+3} \end{bmatrix} \longrightarrow G: H' = \frac{1}{\frac{365}{5(25+3)}} \begin{bmatrix} \frac{65}{25+3} & \frac{-25}{25+3} \\ \frac{45+3}{2(3+25)} & \frac{525+93}{30(25+3)} \end{bmatrix}$$

$$= > G : \begin{bmatrix} \frac{5}{6} & \frac{-5}{18} \\ \frac{5(4S+3)}{72S} & \frac{52S+93}{216S} \end{bmatrix}$$

Kd in
$$V_1 : -I_1 + \frac{V_1 - V_A}{2} + \frac{V_1 - V_2}{2} = 0 \longrightarrow V_1 = \frac{2}{3} V_A + \frac{1}{3} V_2 + I_1$$
 (I)

Kel in V2:
$$\frac{V_2-V_1}{2} + \frac{V_2-V_A}{1} - I_2 = 0 \implies I_2 = \frac{3}{2}V_2 - \frac{1}{2}V_1 - V_A$$
 (III)

$$\frac{\text{CII) in (I)}}{} V_{1} = \frac{2}{3} \left(V_{1} + \frac{1}{3} V_{2} \right) + \frac{1}{3} V_{2} + \overline{L}_{1} = V_{1} \left(1 - \frac{2}{3} \right) = \frac{5}{9} V_{2} + \overline{L}_{1}$$

$$= \sqrt{V_{12} \frac{5}{3} V_{2} + 3I_{1}} , \quad I_{2} = \frac{3}{2} V_{2} - \frac{1}{2} \left(\frac{5}{3} V_{2} + 3I_{1} \right) + V_{1} - \frac{1}{3} V_{2}$$

$$= \times \left[\frac{1}{2} = \frac{1}{3} V_2 - \frac{3}{2} I_1 \right] \qquad H = \left[\frac{3}{3} + \frac{5}{3} \right] \implies G = \frac{1}{2} \left[\frac{1}{3} + \frac{-5}{3} \right]$$

$$\Rightarrow G = \begin{bmatrix} \frac{2}{21} & \frac{-10}{21} \\ \frac{3}{7} & \frac{6}{7} \end{bmatrix}$$