

$$\left\{ \begin{array}{l} \cos(\alpha \pm \beta) = \cos \alpha \cos \beta \mp \sin \alpha \sin \beta \\ \sin(\alpha \pm \beta) = \sin \alpha \cos \beta \pm \sin \beta \cos \alpha \end{array} \right.$$

مکانیک سری هشتم
تاریخ تعلیم:

V. - ۴۱ - ۴۲ - ۴۳ - ۱۹ - ۱۰ - ۱ - ۹ - V - ۴ - ۱ - ۲ - ۳ - ۴ - ۵ - ۶ - ۷ - ۸ - ۹ - ۱۰ - ۱۱ - ۱۲ - ۱۳ - ۱۴ - ۱۵ - ۱۶ - ۱۷ - ۱۸ - ۱۹ - ۲۰ - ۲۱ - ۲۲ - ۲۳ - ۲۴ - ۲۵ - ۲۶ - ۲۷ - ۲۸ - ۲۹ - ۳۰ - ۳۱ - ۳۲ - ۳۳ - ۳۴ - ۳۵ - ۳۶ - ۳۷ - ۳۸ - ۳۹ - ۴۰ - ۴۱ - ۴۲ - ۴۳ - ۴۴ - ۴۵ - ۴۶ - ۴۷ - ۴۸ - ۴۹ - ۵۰ - ۵۱ - ۵۲ - ۵۳ - ۵۴ - ۵۵ - ۵۶ - ۵۷ - ۵۸ - ۵۹ - ۶۰ - ۶۱ - ۶۲ - ۶۳ - ۶۴ - ۶۵ - ۶۶ - ۶۷ - ۶۸ - ۶۹ - ۷۰ - ۷۱ - ۷۲ - ۷۳ - ۷۴ - ۷۵ - ۷۶ - ۷۷ - ۷۸ - ۷۹ - ۸۰ - ۸۱ - ۸۲ - ۸۳ - ۸۴ - ۸۵ - ۸۶ - ۸۷ - ۸۸ - ۸۹ - ۹۰ - ۹۱ - ۹۲ - ۹۳ - ۹۴ - ۹۵ - ۹۶ - ۹۷ - ۹۸ - ۹۹ - ۱۰۰

پس بجهات:

سری:

$$\text{ان) } 2\sin(2t+18^\circ) - 3\cos(2t+35^\circ) + 2 \frac{d^2}{dt^2} \sin(2t-25^\circ)$$

~~پس بجهات~~

$$2 \frac{d^2}{dt^2} \sin(2t-25^\circ) = 2 \frac{d}{dt} 2\cos(2t-25^\circ) = 8\sin(2t-25^\circ)$$

$$= -8\cos(2t-25^\circ-90^\circ) = -8\cos(2t-115^\circ)$$

$$\rightarrow 2\sin(2t+18^\circ) - 3\cos(2t+35^\circ) - 8\cos(2t-115^\circ) = 2\sin 2t \cos 18^\circ$$

$$+ 2\sin 18^\circ \cos 2t - 3\cos 2t \cos 35^\circ + 3\sin 2t \sin 35^\circ - 8\cos 2t \cos 115^\circ$$

$$- 8\sin 2t \sin 115^\circ = 1.9\sin 2t + 0.61\cos 2t - 2.45\cos 2t + 1.72\sin 2t$$

$$+ 3.38\cos 2t - 7.25\sin 2t = 1.54\cos 2t - 3.63\sin 2t =$$

$$\sqrt{(1.54)^2 + (3.63)^2} \cos(2t + \tan^{-1} \frac{3.63}{1.54}) = 3.94 \cos(2t + 66.9^\circ)$$

2.351

$$\text{ب) } \cos 2t + \cos(2t+120^\circ) + \cos(2t+240^\circ) = \cos 2t + \cos 2t \cos 120^\circ$$

$$- \sin 2t \sin 120^\circ + \cos 2t \cos 240^\circ - \sin 2t \sin 240^\circ = \cos 2t - 0.5\cos 2t$$

$$- 0.86\sin 2t - 0.5\cos 2t + 0.86\sin 2t = \cos 2t - \cos 2t = 0$$



$$\text{ا) } \frac{d^2i}{dt^2} + 2\frac{di}{dt} + i = 5\sin(2t + 30^\circ) \rightarrow \omega = 2 \quad : 5 \text{ جر }$$

$$(\cancel{j}\omega)^2 I + 2(\cancel{j}\omega) I + I = 5\cos(2t + 30^\circ - 90^\circ) = 5I - 60$$

$$-4I + 4jI + I = 2.5 - 4.33j \rightarrow (-3 + 4j)I = 2.5 - 4.33j$$

$$\rightarrow I = \frac{2.5 - 4.33j}{-3 + 4j} = \frac{5e^{-60^\circ}}{5e^{126.86^\circ}} \rightarrow |I| = 1, \angle I = -186.86^\circ$$

$$\rightarrow I = \cos(2t - 186.86^\circ)$$

$$\text{ب) } \frac{d^2i}{dt^2} + 3\frac{di}{dt} + 2i = 2\cos(2t - 30^\circ) + 3\sin(2t + 45^\circ) \rightarrow \omega = 2$$

$$2\cos(2t - 30^\circ) + 3\sin(2t + 45^\circ) = 2\cos(2t - 30^\circ) + 3\cos(2t - 45^\circ)$$

$$= (2 \angle -30^\circ) + (3 \angle -45^\circ) = (1.73 - j) + (2.12 - 2.12j) = 3.85 - 3.12j$$

$$-\omega^2 I + 3j\omega I + 2I = -4I^2 + 6jI + 2I = 3.85 - 3.12j$$

$$\rightarrow I = \frac{3.85 - 3.12j}{-2 + 6j} = \frac{4.95 \angle -39^\circ}{6.32 \angle 108.93^\circ} \rightarrow$$

$$|I| = \frac{4.95}{6.32} = 0.78, \angle I = -147.43^\circ \rightarrow I = 0.78 \cos(2t - 147.43^\circ)$$

$$\text{ج) } \frac{d^2i}{dt^2} + 2\frac{di}{dt} + 2i = 2\cos t + 3\sin 2t \rightarrow \text{مطابق لـ 8.2}$$

$$\frac{d^2i_1}{dt^2} + 2\frac{di_1}{dt} + 2i_1 = 2\cos t \rightarrow \omega = 1$$

$$-I_1 + 2jI_1 + 2I_1 = 2 \rightarrow I_1 = \frac{2}{1-2j} = \frac{2 \angle 0^\circ}{2.23 \angle -63.43^\circ} \rightarrow$$



$$|I_1| = 0.89, \angle I_1 = 63.43^\circ \rightarrow i_1 = 0.89 \cos(t + 63.43^\circ)$$

$$\frac{d^2 i_2}{dt^2} + 2 \frac{di_2}{dt} + 2i_2 = 3 \sin 2t = 3 \cos\left(2t - \frac{\pi}{2}\right) \rightarrow \omega = 2$$

$$-4I_2 + 4jI_2 + 2I_2 = -3j \rightarrow I_2 = \frac{-3j}{-2 + 4j} = \frac{3L - 90}{9.47L 116.5}$$

$$\rightarrow |I_2| = 0.67, \angle I_2 = 206.5 \rightarrow i_2 = 0.67 \text{Gs}(2t + 206.5)$$
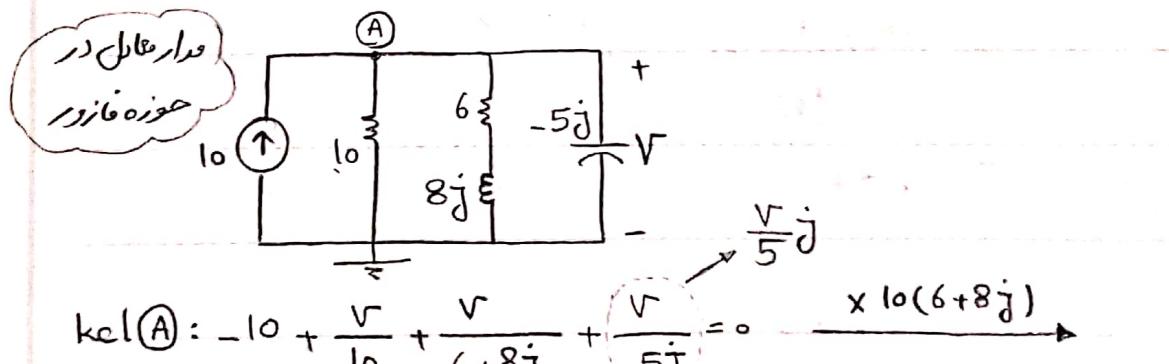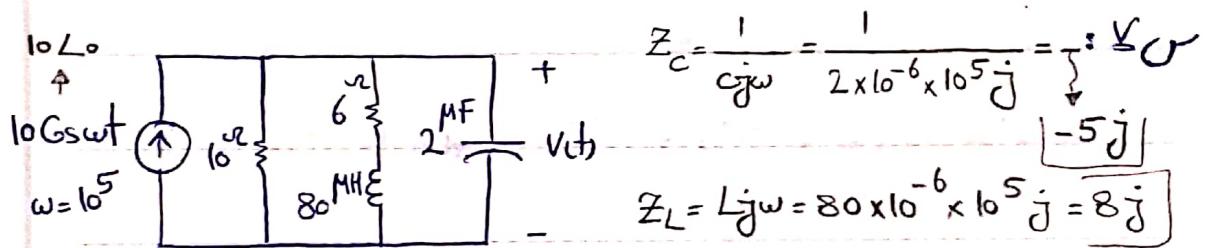
$$\Rightarrow i = i_1 + i_2 = 0.89 \text{Gs}(t + 63.43) + 0.67 \text{Gs}(2t + 206.5)$$



$$kcl(A): -10 + \frac{V}{10} + \frac{V}{6+8j} + \frac{V}{-5j} = 0 \quad \xrightarrow{\times 10(6+8j)}$$


$$(6+8j)V + 10V + 2j(6+8j)V = 100(6+8j) \rightarrow$$

$$(6 + 8j + 10 + 12j - 16)V = 600 + 800j \rightarrow V = \frac{600 + 800j}{20j}$$

$$\rightarrow V = \frac{1000 \angle 53.13}{20 \angle 90} = 50 \angle -36.87$$
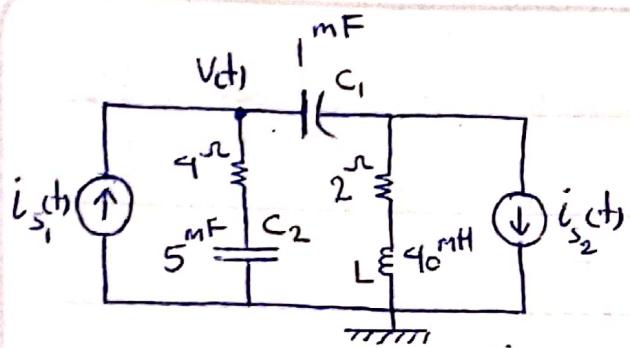
$$V_C(t) = 50 \text{ mV} (10^5 t - 36.87)$$






$$i_{S_1}(t) = C_s I_{00} \omega t \Rightarrow 9 \text{ A}$$

$$i_{S_2}(t) = \frac{1}{2} \sin 100t = \frac{1}{2} C_s (I_{00} \omega - \frac{\pi}{2})$$

$$\omega = 100 \quad = \frac{1}{2} \angle -\frac{\pi}{2} = -\frac{1}{2} j$$

ـ مدار طالب

ـ حوزه مجهول

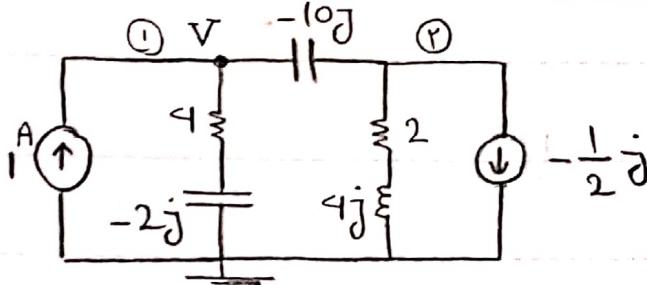

$$Z_L = L j \omega =$$

$$40 \times 10^{-3} \times 100 j = 4 j$$

$$Z_{C_1} = \frac{1}{C_1 j \omega} = \frac{1}{1 \times 10^{-3} \times 100 j} = -10 j, \quad Z_{C_2} = \frac{1}{C_2 j \omega} = \frac{1}{5 \times 10^{-3} \times 100 j} = -2 j$$

$$\text{kel ①: } -1 + \frac{V}{4-2j} + \frac{V-V_2}{-10j} = 0 \rightarrow -10(4-2j) + 10V + j(4-2j)(V-V_2) = 0$$

$$\rightarrow (20j - 40) + (10 + 4j + 2)V = (4j + 2)V_2 \rightarrow$$

$$V_2 = \frac{(-40 + 20j) + (10 + 4j)V}{4j + 2} = \frac{10j + (2 - 2j)V}{4j + 2} \quad \textcircled{*}$$

$$\text{kel ②: } -\frac{1}{2}j + \frac{V_2}{2+4j} + \frac{V_2 - V}{-10j} = 0 \rightarrow$$

$$-5(2+4j)\dot{j} + 10V_2 + j(4+2j)(V_2 - V) = 0 \rightarrow$$

$$(-10j + 20) + (10 + 4j - 2)V_2 + (-4j + 2)V = 0 \rightarrow \textcircled{*}$$

$$(20 - 10j) + (8 + 4j)(10j + (2 - 2j)V) + (2 - 4j)V = 0 \rightarrow$$

$$(20 - 10j + 80j - 40) + (16 - 16j + 8j + 8 + 2 - 4j)V = 0$$


$$\rightarrow (-20 + 70j) + (26 - 12j)V = 0 \rightarrow$$



$$V = \frac{20 - 70j}{26 - 12j} \times \frac{26 + 12j}{26 + 12j} = \frac{520 + 240j - 1820j + 840}{676 + 194}$$

$$= \frac{1360 - 1580j}{820} = 1.65 - 1.92j = 2.53 \angle -49.32$$

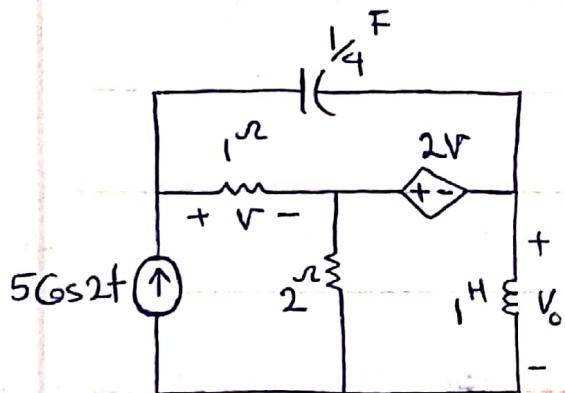$\rightarrow V_{ct} = 2.53 \text{Gs} (100t - 49.32)$




$$\omega = 2$$

$$: \underline{\underline{L}} \omega$$

$$Z_L = Lj\omega = 1 \times 2j = 2j$$
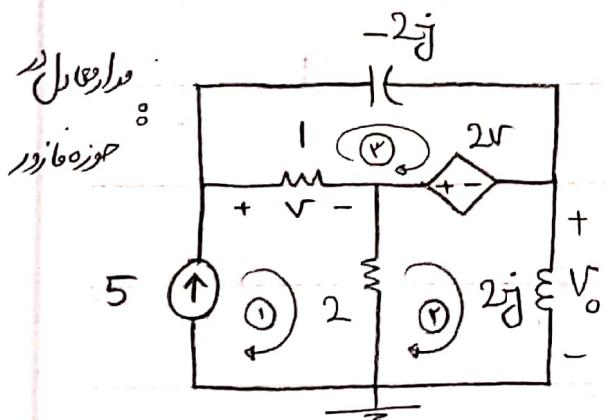
$$Z_C = \frac{1}{Cj\omega} = \frac{1}{\frac{1}{4} \times 2j} = -2j$$



$$I_1 = 5 \text{ A}$$

$$V = I_1 - I_3 = 5 - I_3$$

$$kVL(1): 2(I_2 - 5) + 2(5 - I_3) + (2j)I_2 = 0 \rightarrow$$

$$2I_2 - 10 + 10 - 2I_3 + 2jI_2 = 0 \rightarrow (2 + 2j)I_2 - 2I_3 = 0$$

$$kVL(2): (-2j)I_3 - 2(5 - I_3) + (I_3 - 5) = 0 \rightarrow$$

$$-2jI_3 - 10 + 2I_3 + I_3 - 5 = 0 \rightarrow (3 - 2j)I_3 = 15$$

$$\rightarrow I_3 = \frac{15}{3 - 2j}$$


$$\textcircled{*} \textcircled{*} \text{ in } \textcircled{*} \rightarrow (2 + 2j)I_2 = 2 \left(\frac{15}{3 - 2j} \right)$$



$$\rightarrow I_2 = \frac{30}{3-2j} \times \frac{1}{2+2j} = \frac{30}{6+6j - 4j + 9} = \frac{30}{10+2j}$$

$$V_o = 2j I_2 = 2j \times \frac{30}{10+2j} = \frac{60j}{10+2j} = \frac{60 \angle 90^\circ}{10.19 \angle 11.30^\circ} = 5.88 \angle 78.7^\circ$$

$$V_o(t) = 5.88 \cos(2t + 78.7^\circ)$$

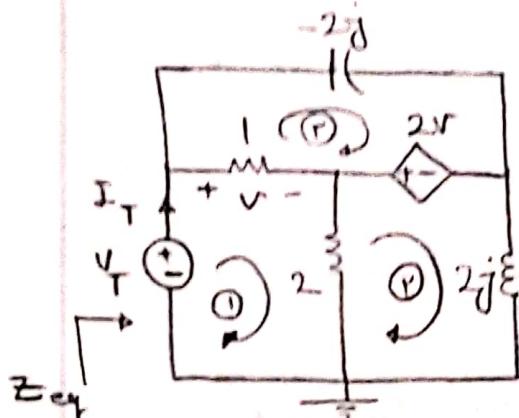

$$KVL \textcircled{I}: -V_T + I_1 - I_3 + 2I_1 - 2I_2 = 0 \quad \textcircled{I}$$

$$KVL \textcircled{II}: 2I_2 - 2I_1 + 2V_T + 2jI_2 = 0$$

$$\rightarrow (2+2j)I_2 - 2I_1 + 2(I_1 - I_3) = 0$$

$$\rightarrow (2+2j)I_2 - 2I_1 + 2I_1 - 2I_3 = 0 \quad \textcircled{II}$$

$$KVL \textcircled{III}: -2jI_3 - 2V_T + I_3 - I_1 = 0 \rightarrow -2jI_3 - 2(I_1 - I_3) + I_3 - I_1 = 0$$

$$\rightarrow (3-2j)I_3 - 3I_1 = 0 \rightarrow I_3 = \frac{3I_1}{3-2j} \quad \textcircled{III}$$

$$\textcircled{III} \text{ in } \textcircled{II} \rightarrow (2+2j)I_2 - 2\left(\frac{3I_1}{3-2j}\right) = 0 \rightarrow I_2 = \frac{6I_1}{(3-2j)(2+2j)}$$

$$\rightarrow I_2 = \frac{6I_1}{10+2j} \quad \textcircled{III}$$

$$\textcircled{I}, \textcircled{III} \text{ in } \textcircled{I} \rightarrow -V_T + 3I_1 - \frac{3I_1}{3-2j} - 2\left(\frac{6I_1}{10+2j}\right) = 0 \rightarrow$$

$$\left(\frac{3(10+2j) - 3(2+2j) - 12}{10+2j} \right) I_1 = V_T \quad \xrightarrow{I_T = I_1}$$



$$Z_{eq} = \frac{V_T}{I_T} = \frac{12}{10+2j} \times \frac{10-2j}{10-2j} = \frac{120-24j}{100+4} = \boxed{1.15 - 0.23j}$$

$$\frac{1}{Cj\omega} = \frac{-j}{2C} = -0.23j$$

$$\rightarrow \frac{1}{w^2 C^2} = \frac{23}{400} \rightarrow C = 2.17$$
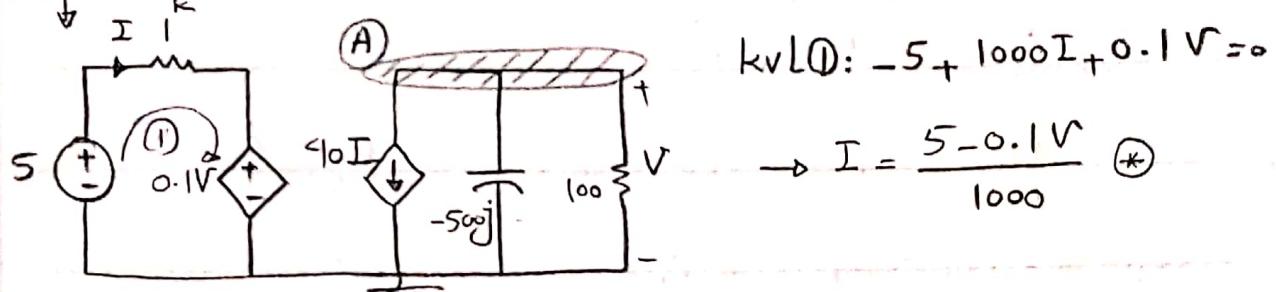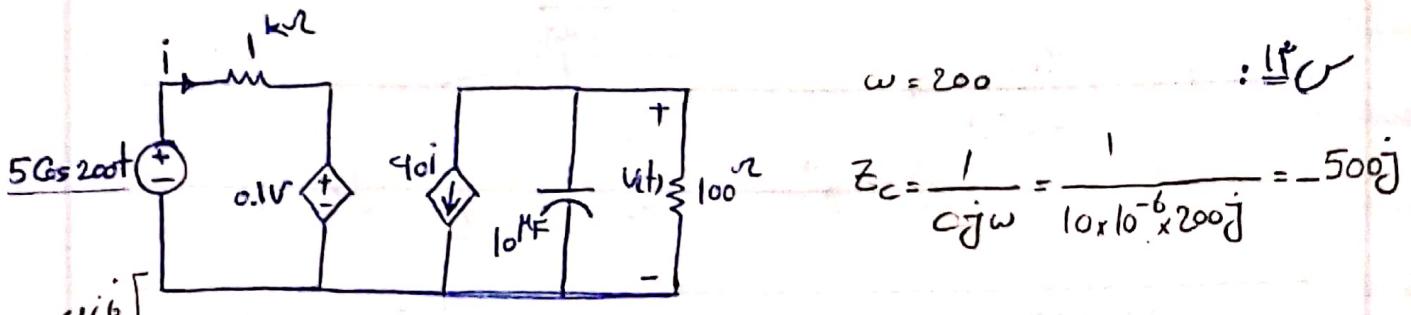
$$Z_{eq} = \frac{1}{1.15 - 0.23j} \quad \boxed{2.17 F}$$







$$kCl \textcircled{3}: 40I + \frac{V}{-500j} + \frac{V}{100} = 0 \textcircled{4} \rightarrow \frac{200 - 4V}{1000} + \frac{V}{500} j + \frac{V}{100} = 0$$

$$\rightarrow 200 - 4V + 2Vj + 10V = 0 \rightarrow (6 + 2j)V = -200 \rightarrow$$

$$V = \frac{-200}{6 + 2j} = \frac{200 \angle 180}{6.32 \angle 18.43} = 31.69 \angle 161.57$$
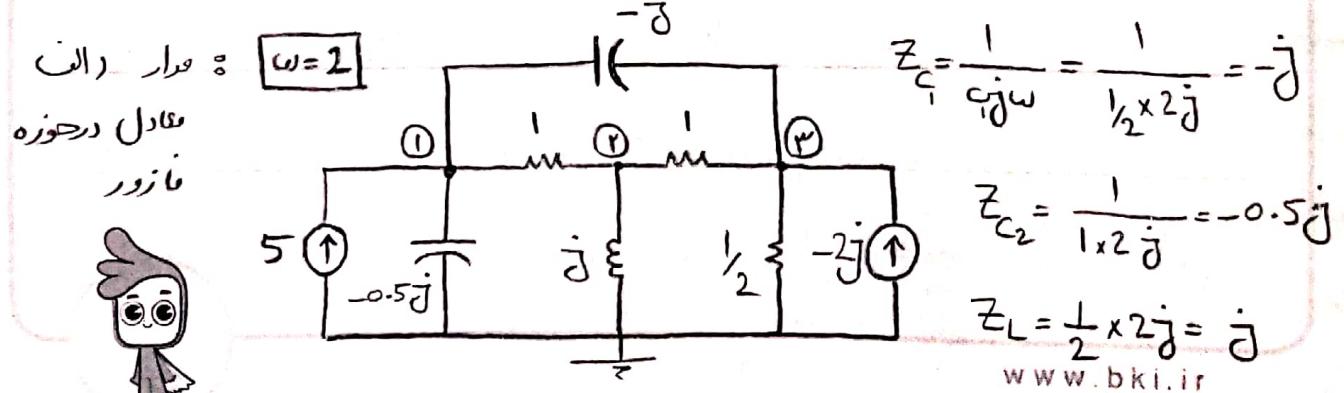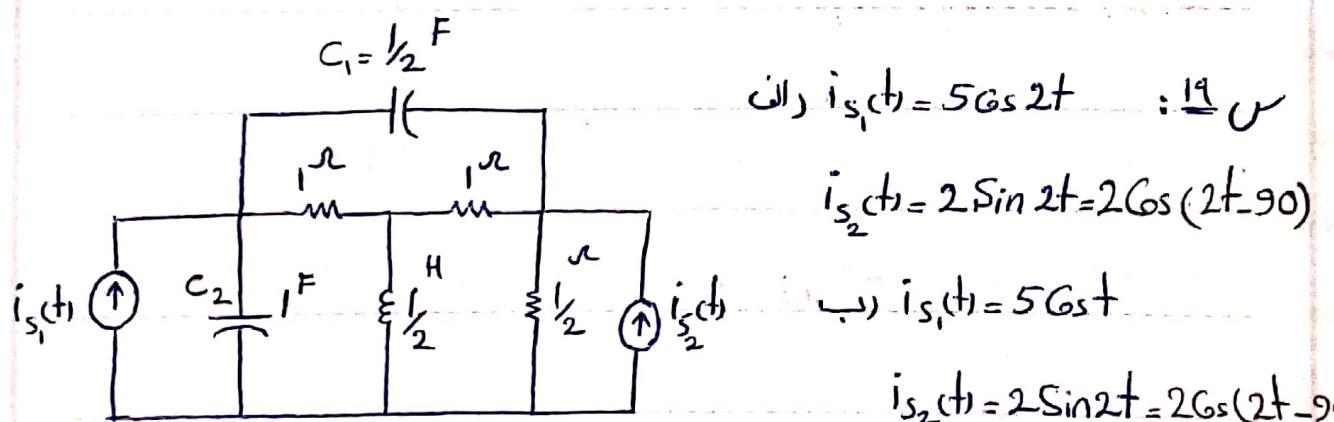
$$V(t) = 31.69 \text{Gs}(200t + 161.57)$$



$$\text{KCL ①: } -5 + \frac{v_1}{-0.5j} + \frac{v_1 - v_2}{1} + \frac{v_1 - v_3}{-j} = 0 \rightarrow$$

$$-5 + 2jv_1 + v_1 - v_2 + jv_1 - jv_3 = 0 \rightarrow (1+3j)v_1 - v_2 - jv_3 = 5 \quad ①$$

$$\text{KCL ②: } \frac{v_2 - v_1}{1} + \frac{v_2 - v_3}{1} + \frac{v_2}{j} = 0 \rightarrow (2-j)v_2 - v_1 - v_3 = 0 \quad ②$$

$$\text{KCL ③: } +2j + \frac{v_3}{1/2} + \frac{v_3 - v_1}{-j} = 0 \rightarrow 2j + 2v_3 + jv_3 - jv_1 = 0 \rightarrow$$

$$(2+j)v_3 - jv_1 = -2j \rightarrow v_1 = \frac{-2j - (2+j)v_3}{-j} = -2j - (2+j)v_3 \quad ③$$

$$\textcircled{*} \text{ in ①} \rightarrow (1+3j)(-2j - (2+j)v_3) - v_2 - jv_3 = 5 \rightarrow$$

$$-2j - 2v_3 - jv_3 + 6 - 6jv_3 + 3v_3 - v_2 - jv_3 = 5 \rightarrow$$

$$v_2 = (1-2j) + (1-8j)v_3 \quad \textcircled{*} \textcircled{**}$$

$$\textcircled{*} \textcircled{**}, \textcircled{**} \text{ in ②} \rightarrow (2-j)((1-2j) + (1-8j)v_3) - (-2j - 2v_3 - jv_3) - v_3 = 0 \rightarrow$$

$$2-4j + 2v_3 - 16jv_3 - j + 2 - jv_3 - 8v_3 + 2j + 2v_3 + jv_3 - v_3 = 0 \rightarrow$$

$$-3j + (-5 - 16j)v_3 = 0 \rightarrow v_3 = \frac{3j}{-5 - 16j}$$

$$\Rightarrow v_1 = -2j - (2+j) \frac{3j}{-5 - 16j} = \frac{-32 + 10j - 6j - 3}{-5 - 16j} = \frac{-35 + 4j}{-5 - 16j}$$


$$v_{C_1} = v_1 - v_3 = \frac{-35 + 4j - 3j}{-5 - 16j} = \frac{-35 + j}{-5 - 16j}$$

ب) بالطريق المضمن في السطر رقم ستاد - انترجع كلام راسينا ومهنيم.

$$\text{حالة اول: } i_{S_1} = 5\cos t \quad \text{حالات: } i_{S_1} = 0$$

$$i_{S_2} = 2\sin 2t$$



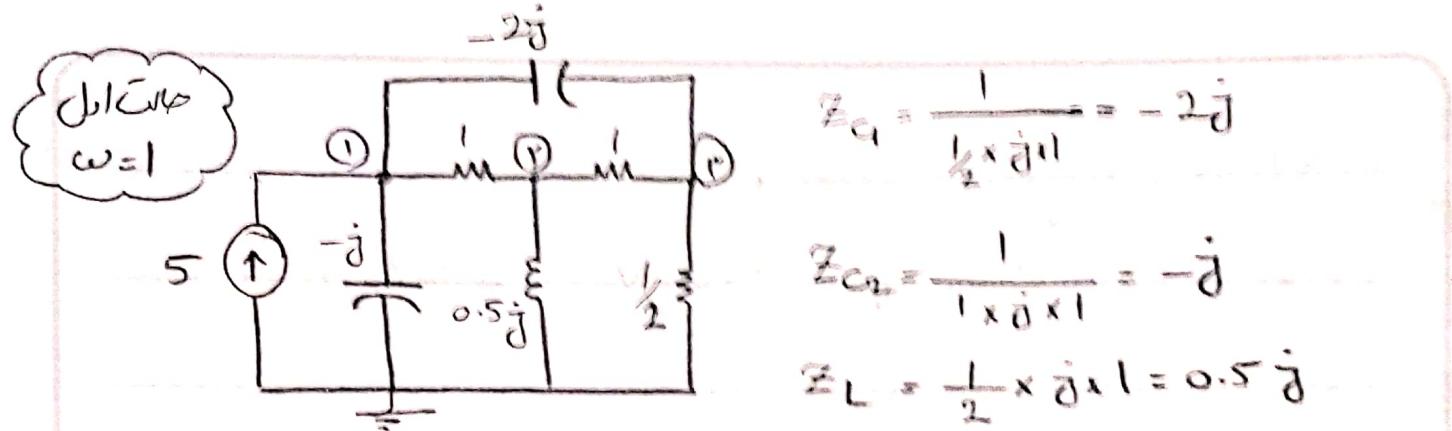


kcl ①:

$$\frac{V_1}{-j} + \frac{V_1 - V_2}{1} + \frac{V_1 - V_3}{-2j} - 5 = 0 \rightarrow 2jV_1 + 2V_1 - 2V_2 + jV_1 - jV_3 - 10 = 0$$

kcl ②:

$$\frac{V_2 - V_1}{1} + \frac{V_2 - V_3}{1} + \frac{V_2}{0.5j} = 0 \rightarrow 2V_2 - V_1 - V_3 - 2jV_2 = 0$$

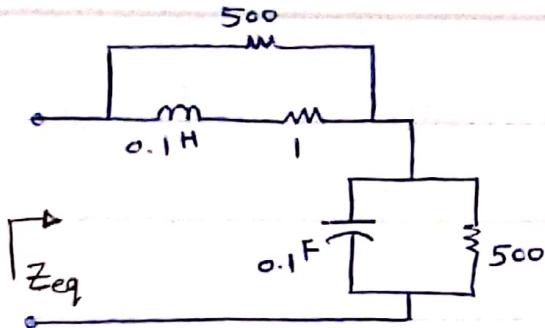kcl ③: $\frac{V_3}{1/2} + \frac{V_3 - V_1}{-2j} + \frac{V_3 - V_2}{1} = 0 \rightarrow 2V_3 + jV_3 - jV_1 + 2V_3 - 2V_2 = 0$




$$Z_L = 0.1 j\omega$$

$\therefore \underline{Z} = \underline{Z}_L$

$$Z_C = \frac{1}{0.1 j\omega} = \frac{10}{j\omega}$$


مدار تماری:

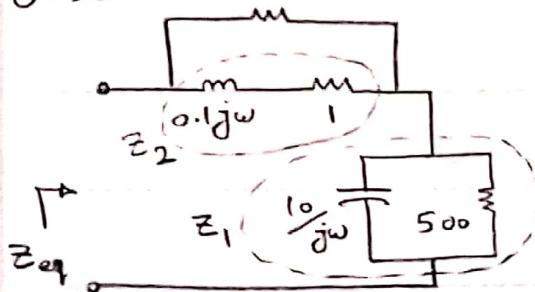

$$Z_1 = \frac{10}{j\omega} \parallel 500 = \frac{\frac{10}{j\omega} \times 500}{\frac{10}{j\omega} + 500} =$$

$$\frac{5 \times 10^3 / j\omega}{10 + 500 j\omega} = \frac{5 \times 10^3}{10 + 500 j\omega} = \frac{500}{1 + 50 j\omega}$$

$$Z_2 = 0.1 j\omega + 1$$

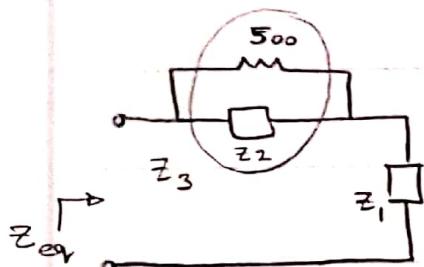

$$Z_3 = Z_2 \parallel 500 = \frac{(0.1 j\omega + 1) 500}{0.1 j\omega + 1 + 500} = \frac{50 j\omega + 500}{0.1 j\omega + 501}$$

$$Z_{eq} = Z_3 + Z_1 = \frac{50 j\omega + 500}{0.1 j\omega + 501} + \frac{500}{1 + 50 j\omega} = \left(\frac{50 j\omega + 500}{0.1 j\omega + 501} \times \frac{501 - 0.1 j\omega}{501 - 0.1 j\omega} \right)$$

$$+ \left(\frac{500}{1 + 50 j\omega} \times \frac{1 - 50 j\omega}{1 - 50 j\omega} \right) = \frac{501(50 j\omega) + 5\omega^2 + 500(501) - 50 j\omega}{(501)^2 + (0.1\omega)^2} +$$

Re Im

$$\frac{500 - 500(50 j\omega)}{1 + (50\omega)^2} = \left[\frac{5\omega^2 + 500(501)}{(501)^2 + (0.1\omega)^2} + \frac{500}{1 + (50\omega)^2} \right] + \left[(50\omega j) \times \right.$$


$$\left. \left(\frac{500}{(501)^2 + (0.1\omega)^2} - \frac{500}{1 + (50\omega)^2} \right) \right]; \quad Im\{Z_{eq}\} = 0 \rightarrow \omega = \underline{\underline{\omega}}$$

$$\frac{500}{(501)^2 + (0.1\omega)^2} - \frac{500}{1 + (50\omega)^2} = 0 \rightarrow 500 \left[(1 + (50\omega)^2) - (501)^2 - (0.1\omega)^2 \right] = 0$$



$$\rightarrow 2500\omega^2 - 251000 = 0 \rightarrow \omega^2 = 100.4 \rightarrow \omega = 10.02$$

مطابق

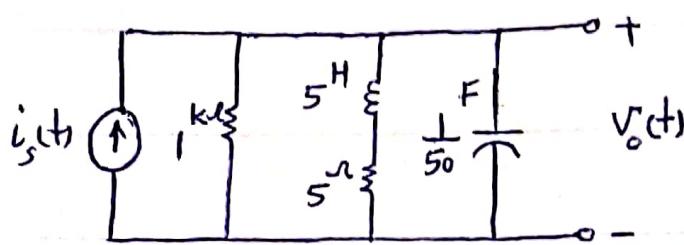

$$i_s(t) = 0.426s\omega t \rightarrow \text{فقط}$$


$$\begin{aligned} Y_1 &= \frac{1}{5j\omega} \parallel \frac{1}{5} = \frac{\frac{1}{5j\omega} \times \frac{1}{5}}{\frac{1}{5j\omega} + \frac{1}{5}} = \frac{1}{25j\omega} \\ Y_{eq} &= \frac{1}{10^{-3} \left| \begin{array}{c|c} 1 & 1 \\ \hline 5j\omega & 5j\omega \end{array} \right|} \parallel \frac{j\omega}{50} = \frac{5j\omega}{25j\omega(1+j\omega)} = \frac{1}{5(1+j\omega)} \end{aligned}$$

$$\begin{aligned} Y_{eq} &= \frac{1}{1000} + \frac{1}{5(1+j\omega)} + \frac{j\omega}{50} = \frac{1+20j\omega}{1000} + \frac{1}{5+5j\omega} \times \frac{5-5j\omega}{5-5j\omega} \\ &= \frac{1+20j\omega}{1000} + \frac{5-5j\omega}{25+25\omega^2} = \frac{(1+20j\omega)(25+25\omega^2) + 1000(5-5j\omega)}{1000(25+25\omega^2)} \end{aligned}$$

$$= \frac{25+25\omega^2 + 500j\omega + 500j\omega^3 + 5000 - 5000j\omega}{1000(25+25\omega^2)}$$

$$\text{Im}\{Y_{eq}\} = \frac{500j\omega(1+\omega^2-10)}{1000(25+25\omega^2)} = 0 \rightarrow \omega^2 - 9 = 0 \rightarrow \omega^2 = 9 \rightarrow \omega = 3$$

$$Y_{eq} \Big|_{\omega=3} = \frac{5250}{25 \times 10^4} = 0.021$$

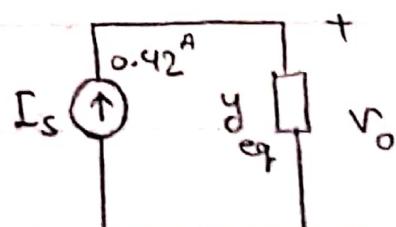


$$V_o = \frac{1}{Y_{eq}} \times I_s = \frac{0.42}{0.021} = 20$$

لأنه في الـ 1000

جزء ثالث مدار دائري زنار تكثيف مكثف (٣ بـ ٢٠١٥، سلطات وسم ٢)

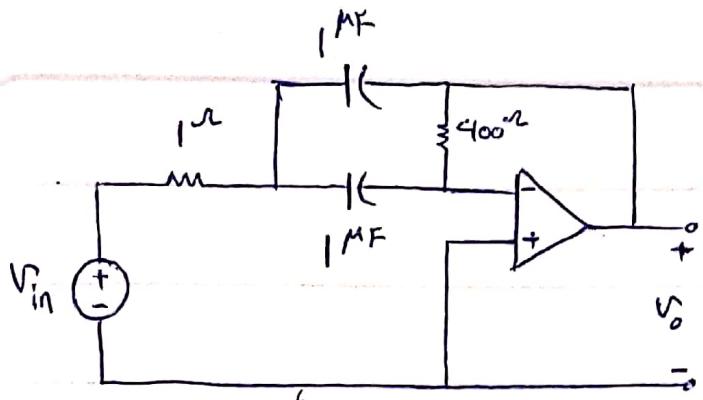
بيان معاينيبيت اكتوبر ٢٠١٥، جواب طالب مهندس محمد كريم





$$H(j\omega) = \frac{V_o}{V_{in}} = ? \quad \text{at } 4\pi \text{ rad/s}$$
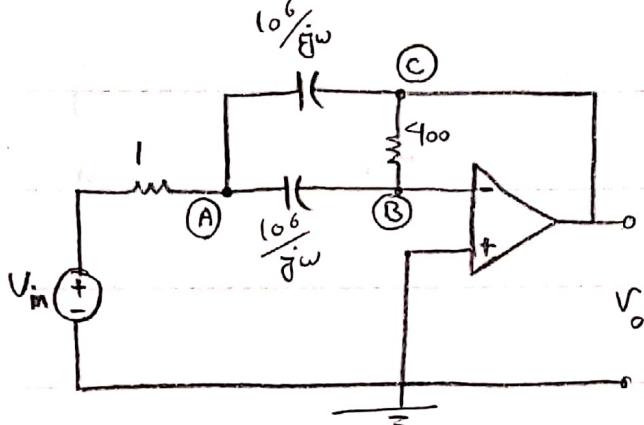
$$Z_c = \frac{1}{10^{-6}j\omega} = \frac{10^6}{j\omega}$$



$$\begin{cases} V_+ = V_- \\ I_- = I_+ = 0 \end{cases}$$

$$V_+ = 0, V_- = V_B$$

$$\boxed{V_B = 0}$$

$$\boxed{V_C = V_o}$$

KCL(A):

$$\frac{V_A - V_{in}}{1} + \frac{V_A - V_C}{10^6/j\omega} + \frac{V_A}{10^6/j\omega} = 0 \rightarrow$$

$$\frac{10^6}{j\omega} (V_A - V_{in}) + V_A - V_o + V_A = 0 \rightarrow (2 - \frac{10^6}{\omega j}) V_A - V_o + \frac{10^6}{\omega j} V_{in} = 0 \quad (I)$$

KCL(B): $\frac{-V_o}{400} + \frac{-V_A}{10^6/j\omega} = 0 \rightarrow (\frac{10^6}{\omega j}) V_o - 400 V_A = 0 \rightarrow$

$$V_A = (\frac{10^6}{400\omega} j) V_o = (\frac{10^4}{4\omega} j) V_o \quad (*)$$

$$(*) \text{ in } (I) \rightarrow (2 - \frac{10^6}{\omega j})(\frac{10^4}{4\omega} j) V_o - V_o + (\frac{10^6}{\omega j}) V_{in} = 0 \rightarrow$$

$$(\frac{10^6}{\omega j}) V_{in} = (1 - \frac{10^{10}}{4\omega^2} - \frac{10^4}{2\omega j}) V_o$$


$$H(j\omega) = \frac{V_o}{V_{in}} = \frac{(10^6/\omega) j}{(\frac{4\omega^2 - 10^{10}}{4\omega^2}) - (\frac{10^4}{2\omega}) j} = \frac{(4 \times 10^6 \omega) j}{(4\omega^2 - 10^{10}) - (2 \times 10^{10} \omega) j}$$




$$|H(j\omega)| = \frac{4 \times 10^6 \omega}{\sqrt{(4\omega^2 - 10^{10})^2 + (2 \times 10^{10} \omega)^2}}$$

$$\angle H(j\omega) = \frac{\pi}{2} - \tan^{-1} \left(\frac{2 \times 10^{10} \omega}{4\omega^2 - 10^{10}} \right)$$

$\left\{ \begin{array}{l} \text{if } \omega = 0 \rightarrow |H(j\omega)| = 0 ; \quad \text{if } \frac{d|H(j\omega)|}{d\omega} = 0 \rightarrow |H(j\omega)| = \text{Max} \\ \text{if } \omega = \infty \rightarrow |H(j\omega)| = 0 \end{array} \right.$
 $\delta \omega_0 = \text{فرکانس کریکت}$

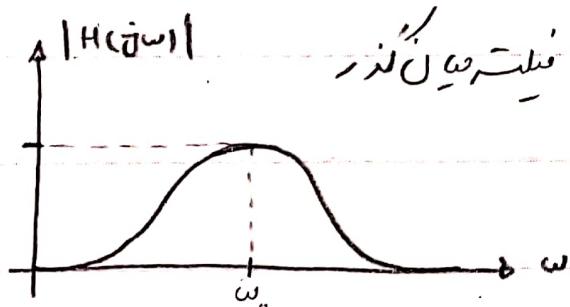

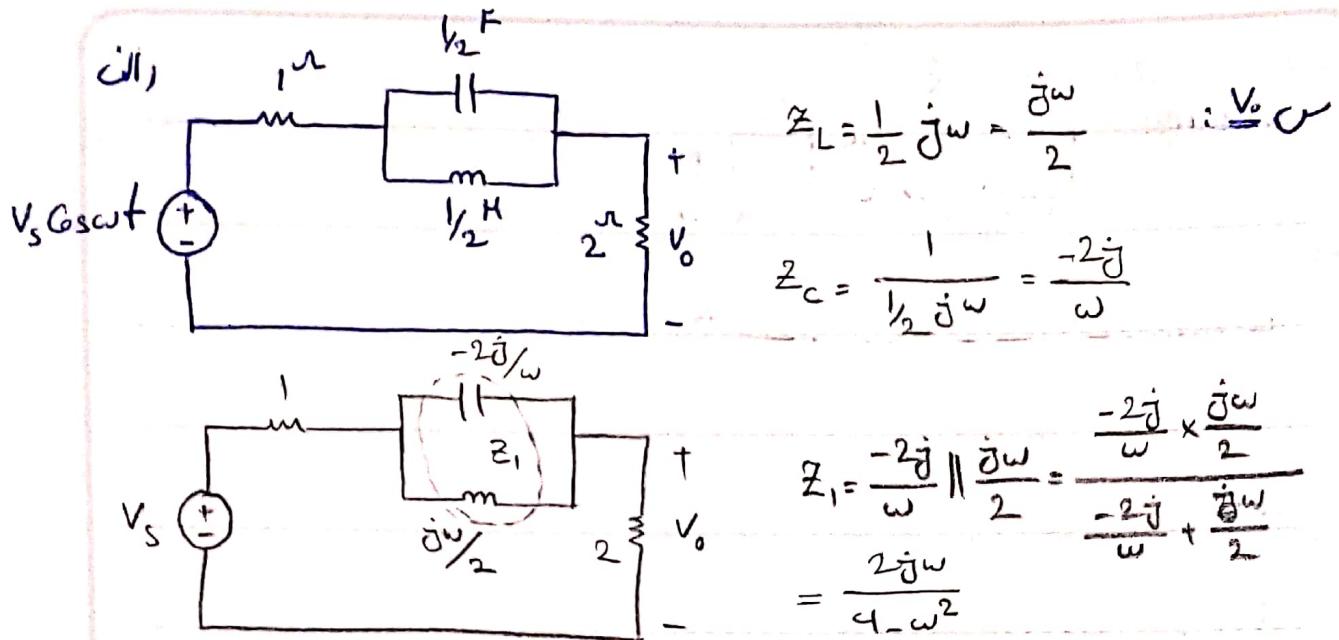


ω تسلیمان \rightarrow تسلیمان

$$V_o = \frac{2}{1 + 2 + \frac{2j\omega}{4 - \omega^2}} \times V_s \rightarrow \frac{V_o}{V_s} = \frac{2}{3 + \frac{2j\omega}{4 - \omega^2}} = \frac{2(4 - \omega^2)}{12 - 3\omega^2 + 2j\omega}$$

$$\rightarrow H(j\omega) = \frac{8 - 2\omega^2}{12 - 3\omega^2 + 2j\omega} \rightarrow |H(j\omega)| = \frac{8 - 2\omega^2}{\sqrt{(12 - 3\omega^2)^2 + (2j\omega)^2}}$$

$$\left\{ \begin{array}{l} \text{if } \omega = 0 \rightarrow |H(j\omega)| = \frac{2}{3} ; \quad \text{if } |H(j\omega)| = 0 \rightarrow \omega_0 = \omega_{\text{ذرو}} \\ \text{if } \omega = \infty \rightarrow |H(j\omega)| = \frac{2}{3} \quad \rightarrow 8 - 2\omega^2 = 0 \rightarrow \omega^2 = 4 \rightarrow \omega_0 = 2 \end{array} \right.$$

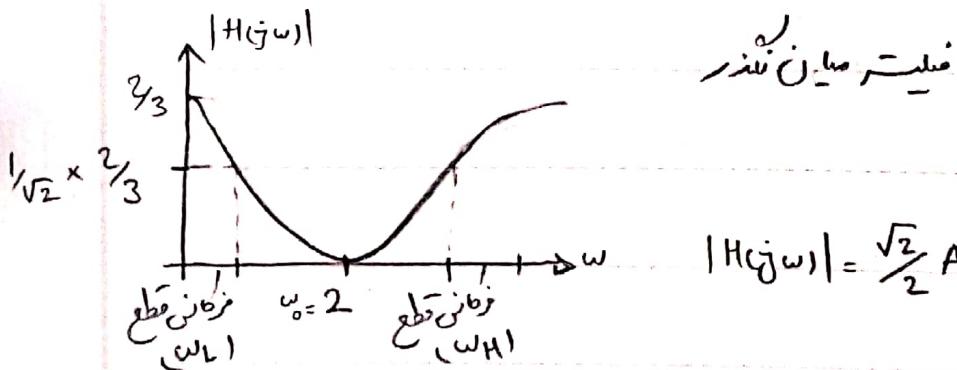


فرطان وضع

$$|H(j\omega)| = \frac{\sqrt{2}}{2} A_{\max} = \frac{\sqrt{2}}{2} \times \frac{2}{3} = \frac{\sqrt{2}}{3}$$
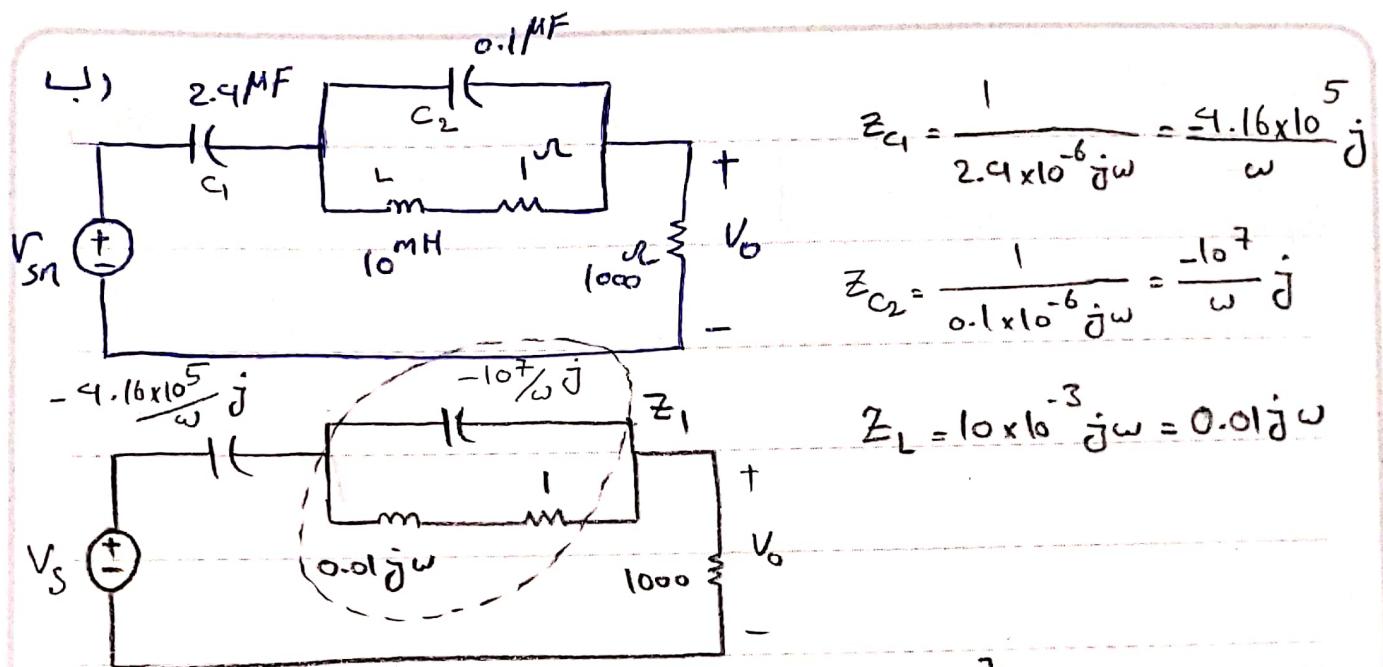
$$\rightarrow \frac{8 - \omega^2}{\sqrt{(12 - 3\omega^2)^2 + 4\omega^2}} = \frac{\sqrt{2}}{3} \rightarrow \left\{ \begin{array}{l} \omega_L = 1.69 \\ \omega_H = 2.36 \end{array} \right.$$





$$Z_{C_1} = \frac{1}{2.4 \times 10^{-6} j\omega} = \frac{4.16 \times 10^5}{\omega} j$$

$$Z_{C_2} = \frac{1}{0.1 \times 10^{-6} j\omega} = \frac{-10^7}{\omega} j$$

$$Z_L = 10 \times 10^{-3} j\omega = 0.01 j\omega$$

$$Z_1 = (1 + 0.01 j\omega) \parallel \left(\frac{-10^7}{\omega} j \right) = \frac{(1 + 0.01 j\omega) \left(\frac{-10^7}{\omega} j \right)}{1 + 0.01 j\omega + \frac{-10^7}{\omega} j} = \frac{-10^7 j + 10^5 \omega}{-10^7 j + \omega + 10^{-2} j\omega^2}$$

مقدمة في الميكانيكا (القسم الثاني)

$$\frac{V_o}{V_s} = \frac{1000}{1000 + \frac{-4.16 \times 10^5}{\omega} j + \frac{-10^7 j + 10^5 \omega}{-10^7 j + \omega + 10^{-2} j\omega^2}} =$$

مقدار عایق کلی: 9Ω , 1 , 1

مقدار سری فاز


$114 - 11 - 0V - 0V - 0V - 0V$: مجموع فاز

$22 - 21 - 12 - 11$: مجموع فاز

$14 - 19 - 19$: مجموع فاز

نسبت

$5G_{S2000f}$

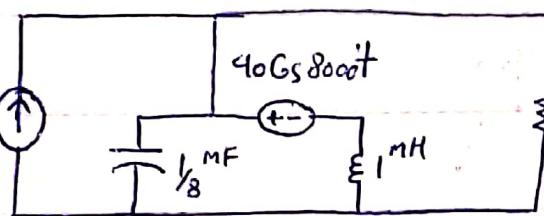


$$P_R = \frac{VI}{2} = \frac{RI^2}{2}$$

: $\underline{\underline{U}}$

لطفاً

کلی

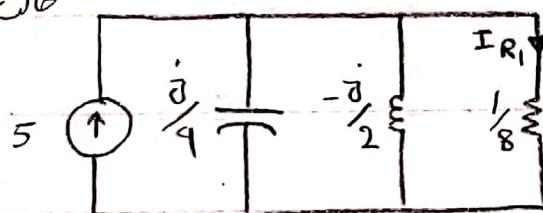


$$y_C = \frac{1}{8} \times 10^{-3} \times 2 \times 10^3 j = \frac{1}{4} j$$

$$y_L = \frac{1}{1 \times 10^{-3} \times 2 \times 10^3 j} = -0.5 j$$

$$\text{کلی: } I_{R1} = \frac{\frac{1}{8}}{\frac{1}{8} + \frac{j}{4} - \frac{j}{2}} \times 5 = \frac{1}{1 + 2j - 4j} \times 5 = \frac{5}{1 - 2j} = \frac{5L}{2.23L - 63.513}$$

کلی

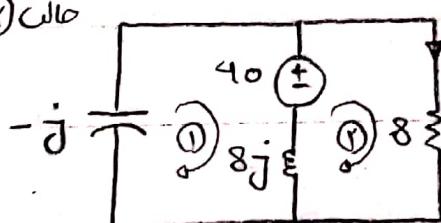

$$\text{kvl ①: } -jI_1 + 40 + 8jI_1 - 8jI_2 = 0$$

$$\rightarrow 40 + 7jI_1 - 8jI_2 = 0 \rightarrow I_1 = \frac{-40 + 8jI_2}{7j}$$

$$\text{kvl ②: } 8jI_2 - 8jI_1 - 40 + 8I_2 = 0 \rightarrow (8 + 8j)I_2 - 8jI_1 = 40$$


$$\rightarrow (8 + 8j)I_2 + \frac{320}{7} - \frac{64jI_2}{7} = 40 \rightarrow (8 - 1.14j)I_2 = -5.71$$

$$\rightarrow I_2 = I_{R2} = \frac{-5.71}{8 - 1.14j} = \frac{5.71 \angle 180}{8.08 \angle 8.11}$$





$$I_R = I_{R_1} + I_{R_2} \rightarrow |I_R| = |I_{R_1}| + |I_{R_2}| = 2.29 + 0.69 = 2.88$$

$$P_{R_{avg}} = \frac{R |I|^2}{2} = \frac{8 (2.88)^2}{2} = 4 \times 8.29 = \underline{\underline{33.16}}$$

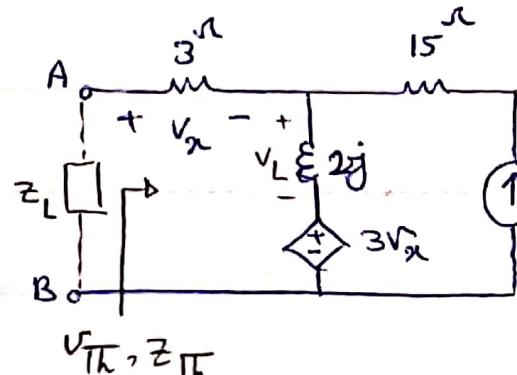

at or

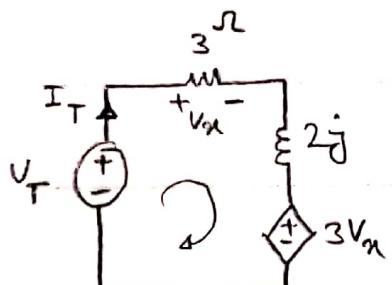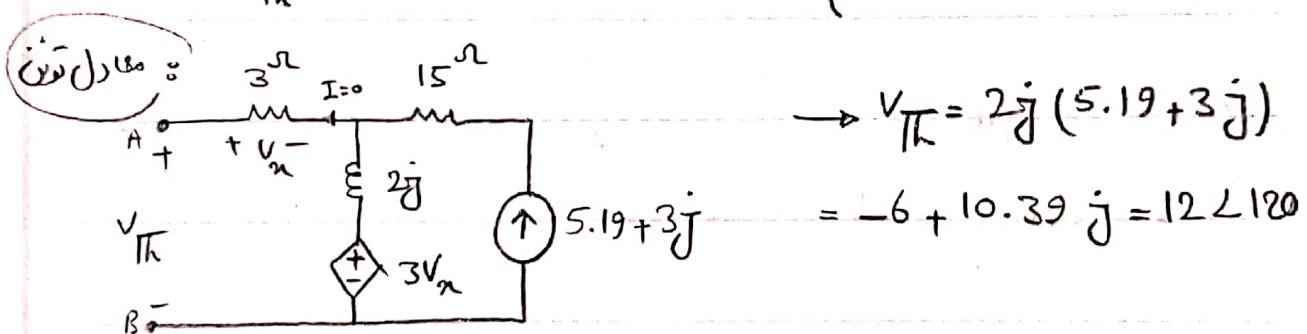
$$\begin{cases} V_{Th} = V_L + 3V_x \\ V_L = Z_L(I) \end{cases}$$



$$kvl: -V_T + 3I_T + 2jI_T + 3V_x = 0$$

$$(3 + 2j)I_T + 3(3I_T) = V_T \rightarrow$$
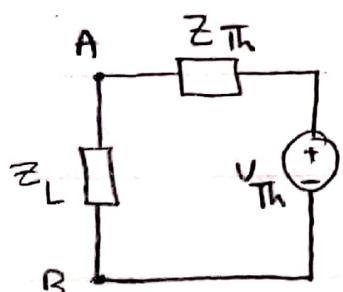
$$(12 + 2j)I_T = V_T \rightarrow Z_{Th} = \frac{V_T}{I_T} = 12 + 2j$$



$$\boxed{Z_L = Z_{Th}} \rightarrow Z_L = \underline{\underline{12 - 2j}}$$

With $V_{AB} = \frac{Z_L}{Z_L + Z_{Th}} \times V_{Th}$

$$= \frac{12 - 2j}{24} \times (-6 + 10.39j) = \frac{-72 + 124.68j + 12j + 20.78}{24}$$


$$= \frac{-51.22 + 136.68j}{24} = -2.13 + 5.7j = 6 \angle 110.5$$



$$I_{AB} = \frac{V_{AB}}{Z_L} = \frac{-2.13 + 5.7j}{12 - 2j} = \frac{6 \angle 110.5^\circ}{12.16 \angle -9.5^\circ} = 0.5 \angle 120^\circ$$

$$P_{AB_{\max}} = \frac{|V_{AB}| |I_{AB}|}{2} G_s (\Phi_{V_{AB}} - \Phi_{I_{AB}}) = \frac{6(0.5)}{2} G_s (110.5 - 120)$$

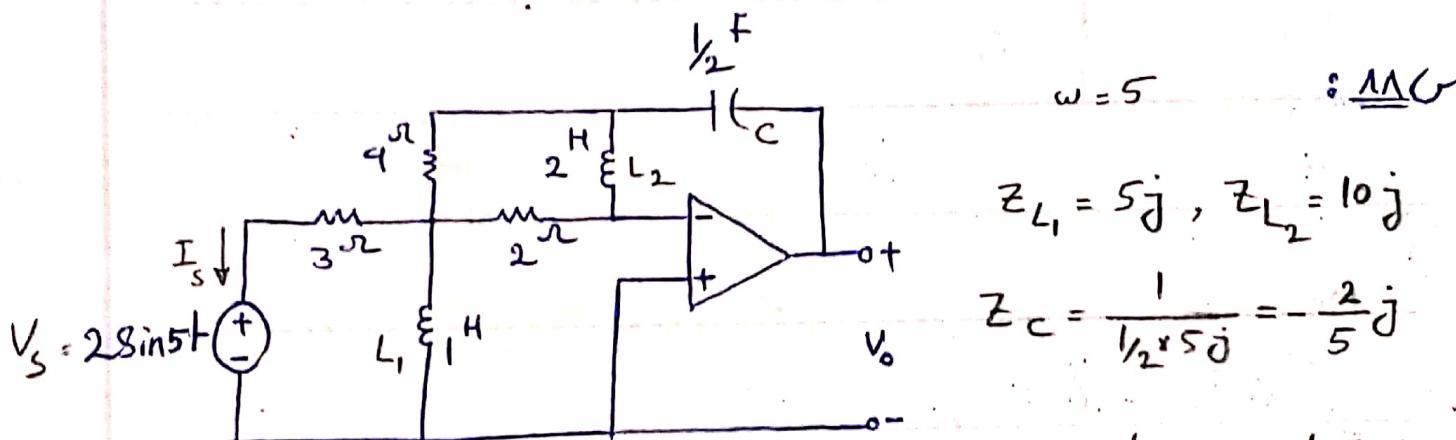
$$= 1.5 G_s (-9.5) = 1.5 \times 0.98 = 1.47$$



$$Z_{L_1} = 5j, Z_{L_2} = 10j$$

$$Z_C = \frac{1}{1/2 \times 5j} = -\frac{2}{5}j$$
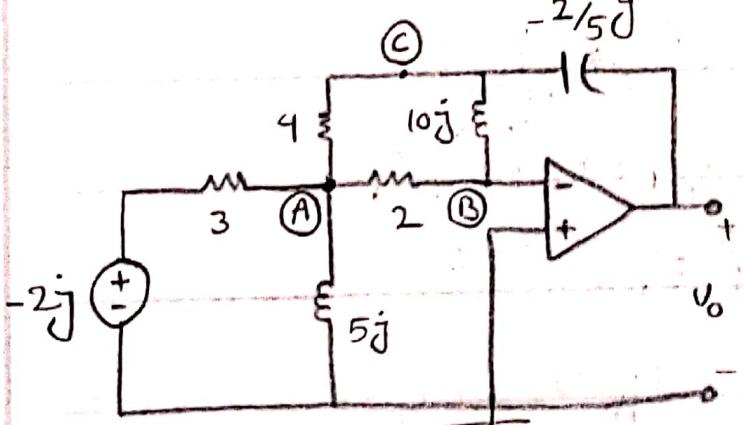
$$V_s = 28 \sin 5t = 2G_s (5t - 90^\circ) = -2j$$



$$\text{KCL } \textcircled{A}: \frac{V_A + 2j}{3} + \frac{V_A}{5j} + \frac{V_A - V_C}{4} + \frac{V_A}{2} = 0 \rightarrow$$

$$20V_A + 40j - 12jV_A + 15V_A - 15V_C + 30V_A = 0 \rightarrow$$

$$(65 - 12j)V_A + 40j = 15V_C \quad \textcircled{**}$$

$$\text{KCL } \textcircled{B}: \frac{-V_A}{2} + \frac{-V_C}{10j} = 0 \rightarrow -5V_A + V_C = 0 \rightarrow V_C = 5V_A \quad \textcircled{*}$$



$$\text{KCL at C: } \frac{V_C - V_A}{4} + \frac{V_C}{10j} + \frac{V_C - V_o}{-2/5j} = 0 \rightarrow 5V_C - 5V_A - 2jV_C + 50jV_C - 50jV_o = 0$$

$$\rightarrow (5 + 48j)V_C - 5V_A = 50jV_o \quad \textcircled{*} \rightarrow (25 + 240j - 5)V_A = 50jV_o$$

$$(20 + 240j)V_A = 50jV_o \rightarrow V_o = \frac{2 + 24j}{5}V_A \quad \textcircled{1}$$

$$\textcircled{*} \text{ in } \textcircled{*} \quad (65 - 12j)V_A + 40j = 75V_A \rightarrow (10 + 12j)V_A = 40j \rightarrow$$

$$V_A = \frac{40j}{10 + 12j} \quad \textcircled{2}$$

$$\textcircled{2} \text{ in } \textcircled{1} \rightarrow V_o = \frac{2 + 24j}{5} \times \frac{\frac{40j}{10 + 12j}}{10 + 12j} = \frac{(1 + 12j)(8j)}{5 + 6j} = \frac{-96 + 8j}{5 + 6j}$$

$$V_o = \frac{96.3 \angle 175.2}{7.8 \angle 50.2} = 12.34 \angle 125 \rightarrow V_o = -7 + 10.1j$$

$$V_o(t) = 12.34 \cos(5t + 125)$$

$$V_S = -2j = 2 \angle -90$$

$$I_S = \frac{V_A - V_S}{3} = \frac{\frac{40j}{10 + 12j} + 2j}{3} = \frac{1.9 + 1.6j + 2j}{3} = \frac{1.9 + 3.6j}{3} \rightarrow$$


$$I_S = 0.63 + 1.2j = 1.3 \angle 62.3$$

$$P_S = \frac{V_S I_S}{2} \cos(\Phi_{V_S} - \Phi_{I_S}) = \frac{2 \times 1.3}{2} \cos(-90 - 62.3) = -1.14$$

$$Q_S = \frac{V_S I_S}{2} \sin(\Phi_{V_S} - \Phi_{I_S}) = \frac{2 \times 1.3}{2} \sin(-90 - 62.3) = -0.59 \quad \text{VAR}$$
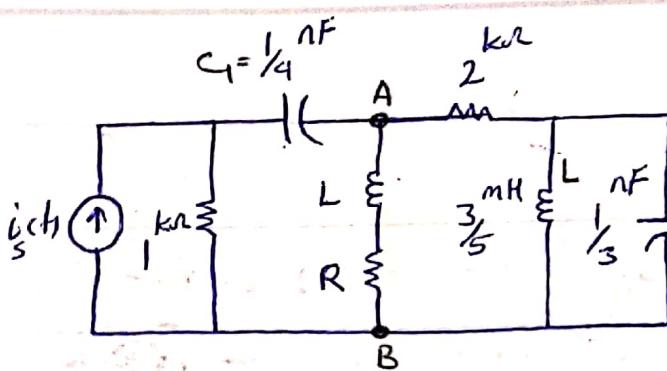
$$\text{مكمل} S_S = P_S + jQ_S = -1.14 - 0.59j \quad \text{VA}$$






$$i_s(t) = 56s 2 \times 10^6 t \text{ mA} : 04 \text{ C}$$

$$\omega = 2 \times 10^6$$

$$Z_L = \frac{3}{5} \times 10^{-3} \times 2 \times 10^6 j = \frac{6}{5} \times 10^3 j$$
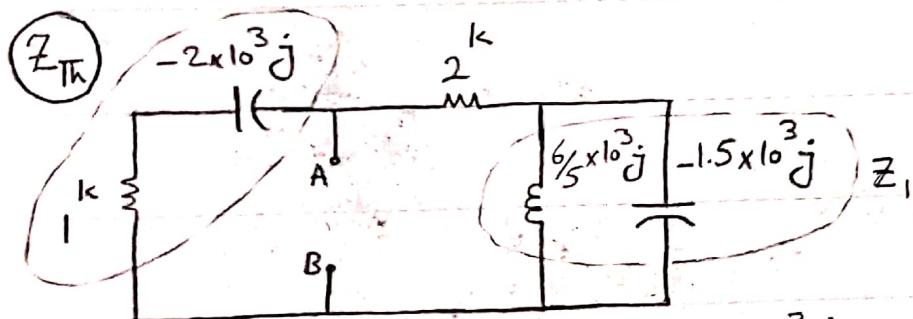
$$Z_{C_1} = \frac{1}{\frac{1}{4} \times 10^{-9} \times 2 \times 10^6 j} = -2 \times 10^3 j, Z_{C_2} = \frac{1}{\frac{1}{3} \times 10^{-9} \times 2 \times 10^6 j} = -1.5 \times 10^3 j$$




$$Z_1 = \left(\frac{6}{5} \times 10^3 j \right) \parallel \left(-1.5 \times 10^3 j \right) = \frac{(6/5 \times 10^3 j)(-1.5 \times 10^3 j)}{(6/5 \times 10^3 j) + (-1.5 \times 10^3 j)} = \frac{1.8 \times 10^6}{-0.3 \times 10^3 j} = 6 \times 10^3$$

$$Z_2 = Z_1 + 2 = 6 \times 10^3 + 2 \times 10^3 = 8 \times 10^3, Z_3 = 10^3 - 2 \times 10^3 j$$

$$Z_{Th} = Z_2 \parallel Z_3 = (8 \times 10^3) \parallel (10^3 - 2 \times 10^3 j) = \frac{8 \times 10^3 (10^3 - 2 \times 10^3 j)}{8 \times 10^3 + 10^3 - 2 \times 10^3 j}$$
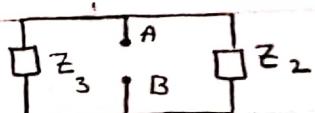
$$= \frac{8 \times 10^6 (1 - 2j)}{10^3 (9 - 2j)} = \frac{8 \times 10^3 (1 - 2j)}{9 - 2j} \times \frac{9 + 2j}{9 + 2j}$$



$$= \frac{8 \times 10^3 (9 + 2j - 18j + 9)}{81 + 9} = \frac{(13 - 16j) 8 \times 10^3}{85} = (1.22 - 1.5j) \times 10^3$$

$$Z_L = Z_{AB} = \overline{Z_{Th}} = 1.22 + 1.5j = Z_R + Z_L \rightarrow R = 1.22$$

$$L \omega = 1.5j \rightarrow 2 \times 10^6 L = 1.5 \rightarrow L = 0.75 \times 10^{-6} = 0.75 \mu H$$